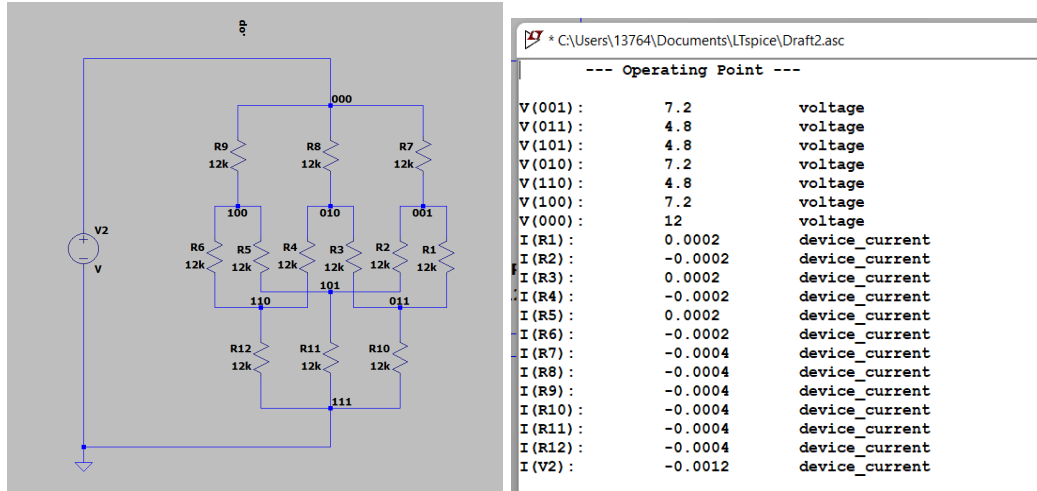



## Part 1: DC Analysis

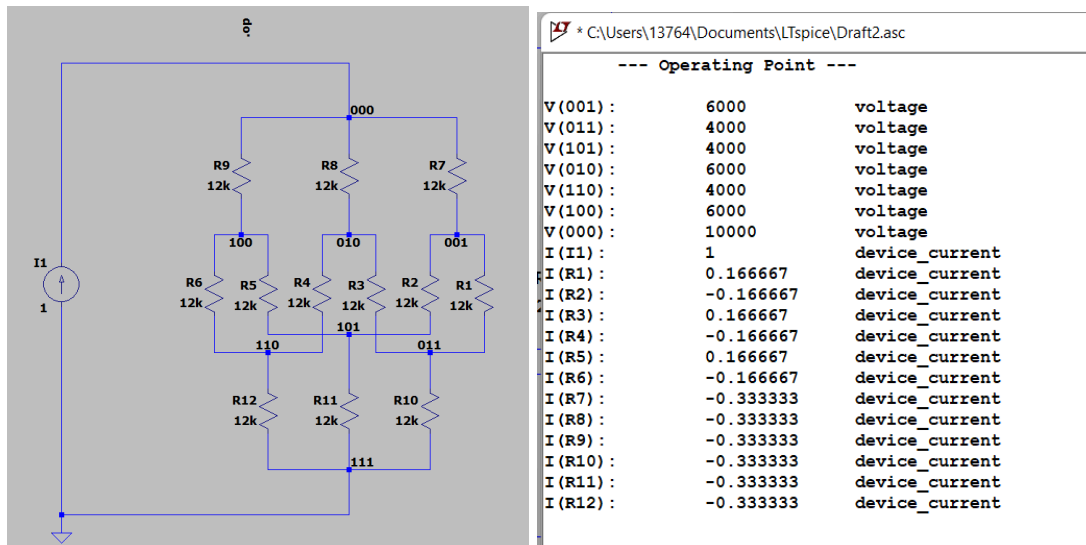- a. The cubic circuit is flattened into the diagram below, with the nodes labeled. I connected a 12V voltage source across the terminals. Below are the diagram and .op simulation results:




Using Ohm's Law,  $R_{eq} = \frac{v_{v2}}{i_{v2}} = \frac{12V}{0.0012A} = 1k\Omega$ .

Similarly, I drove the terminals with a 1A current source and measured the voltage across the current source. They produce the same results.




$R_{eq} = \frac{v_{000} - 0}{i_{I1}} = \frac{10000V}{1A} = 1k\Omega$ .

b.  $P_{R1} = I(R1) * V(vout)$ .

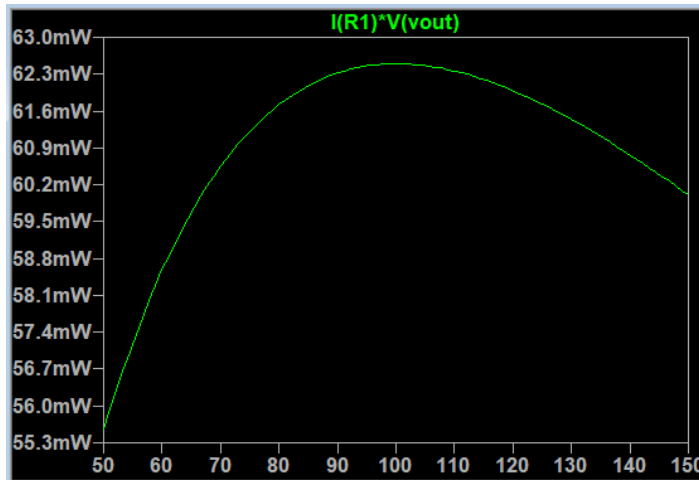

The shape is an upside-down curve, with a maximum at  $R_{load} = 100\Omega$ . If  $R_{load}$  is too low, most voltage will be wasted by  $R_2$ . If  $R_{load}$  is too high, less current will pass through the series circuit, decreasing the power. Since power is the product of voltage and current, the curve is bell-shaped, with a maximum occurring when  $R_{load} = R_2$ .


c. .dc Vin -4 4 0.01

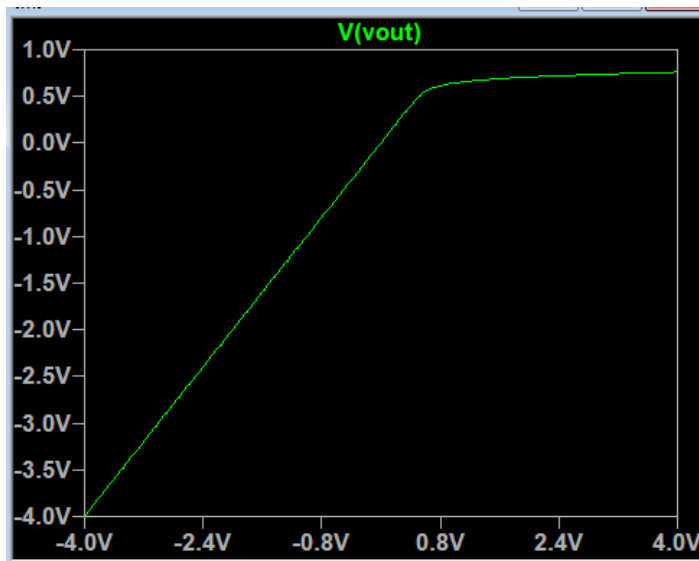

At approximately  $V_{in} < 0.6 V$ ,  $V_{out} = V_{in}$ . Once  $V_{in} > 0.6 V$ ,  $V_{out}$  caps at 0.6 V. Therefore, the transfer curve is initially linear but flattens for positive  $V_{in}$ .

## Part 2: Transient Analysis


a.  $V_{in} = 1\text{ V}$  (peak)

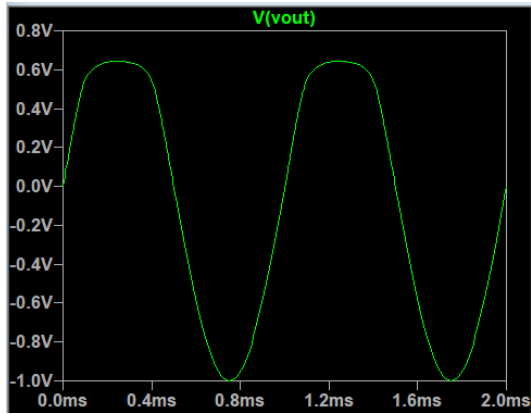

Harmonic Number	Frequency [Hz]	Fourier Component	Normalized Component	Phase [degree]	Normalized Phase [deg]
1	1.000e+3	8.683e-1	1.000e+0	90.01°	0.00°
2	2.000e+3	9.565e-2	1.102e-1	0.10°	-89.90°
3	3.000e+3	5.249e-2	6.045e-2	89.75°	-0.26°
4	4.000e+3	1.638e-2	1.887e-2	-178.98°	-268.99°
5	5.000e+3	3.384e-3	3.898e-3	93.30°	3.30°
6	6.000e+3	8.331e-3	9.594e-3	178.89°	88.89°
7	7.000e+3	4.320e-3	4.975e-3	-90.41°	-180.42°
8	8.000e+3	1.727e-4	1.989e-4	133.94°	43.93°
9	9.000e+3	2.740e-3	3.156e-3	-85.15°	-175.15°
10	1.000e+4	1.473e-3	1.696e-3	-6.05°	-96.06°
11	1.100e+4	8.400e-5	9.674e-5	-81.91°	-171.91°
12	1.200e+4	8.053e-4	9.274e-4	-10.48°	-100.49°
13	1.300e+4	8.966e-4	1.033e-3	101.74°	11.74°
14	1.400e+4	3.753e-5	4.322e-5	36.63°	-53.38°
15	1.500e+4	4.292e-4	4.943e-4	94.86°	4.85°
16	1.600e+4	2.500e-4	2.879e-4	161.53°	71.53°
17	1.700e+4	5.501e-6	6.335e-6	-61.67°	-151.67°
18	1.800e+4	1.571e-4	1.809e-4	170.48°	80.48°
19	1.900e+4	1.391e-4	1.601e-4	-107.02°	-197.02°
20	2.000e+4	2.419e-5	2.786e-5	70.38°	-19.62°


Partial Harmonic Distortion: 12.764093%  
Total Harmonic Distortion: 12.764113%

$V_{in} = 0.2\text{ V}$  (peak)

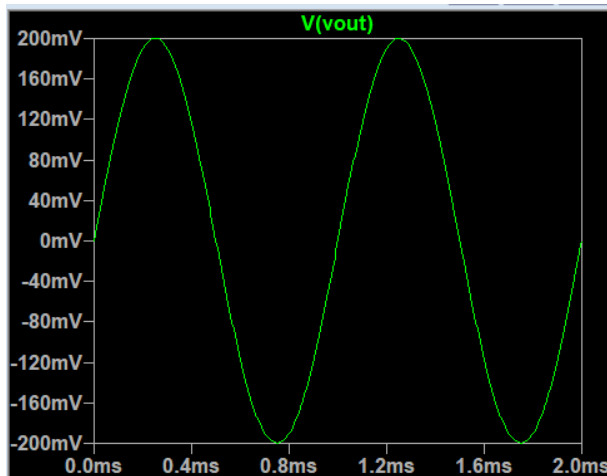


Partial Harmonic Distortion: 0.110740%  
Total Harmonic Distortion: 0.111266%

$V_{in} = 2\text{ V}$  (peak)

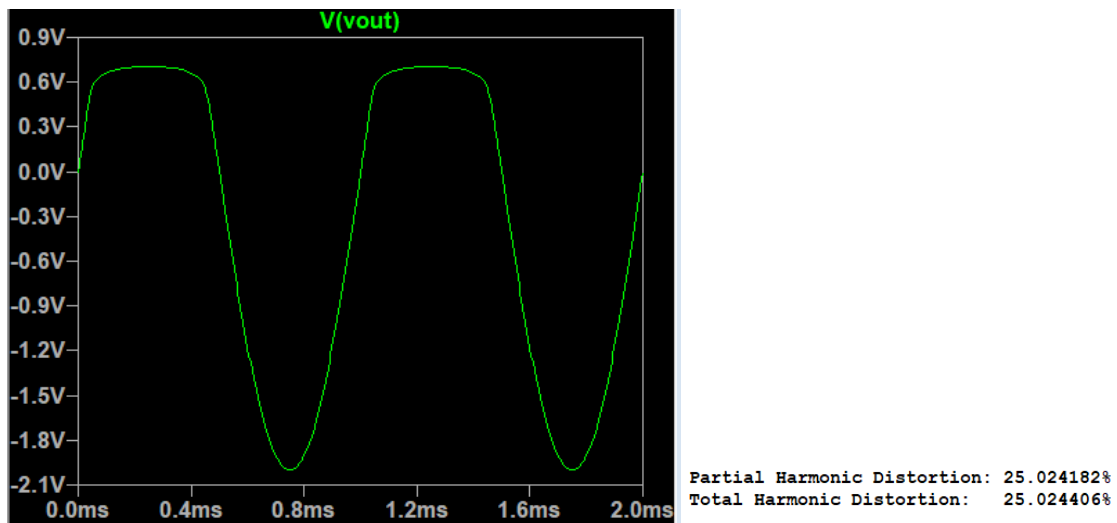

The diode cuts off all the positive half of  $V_{in}$  and caps it at about 0.7 V. The higher the  $V_{in}$  peak, the more the distortion, as shown in the Fourier analysis.


b.

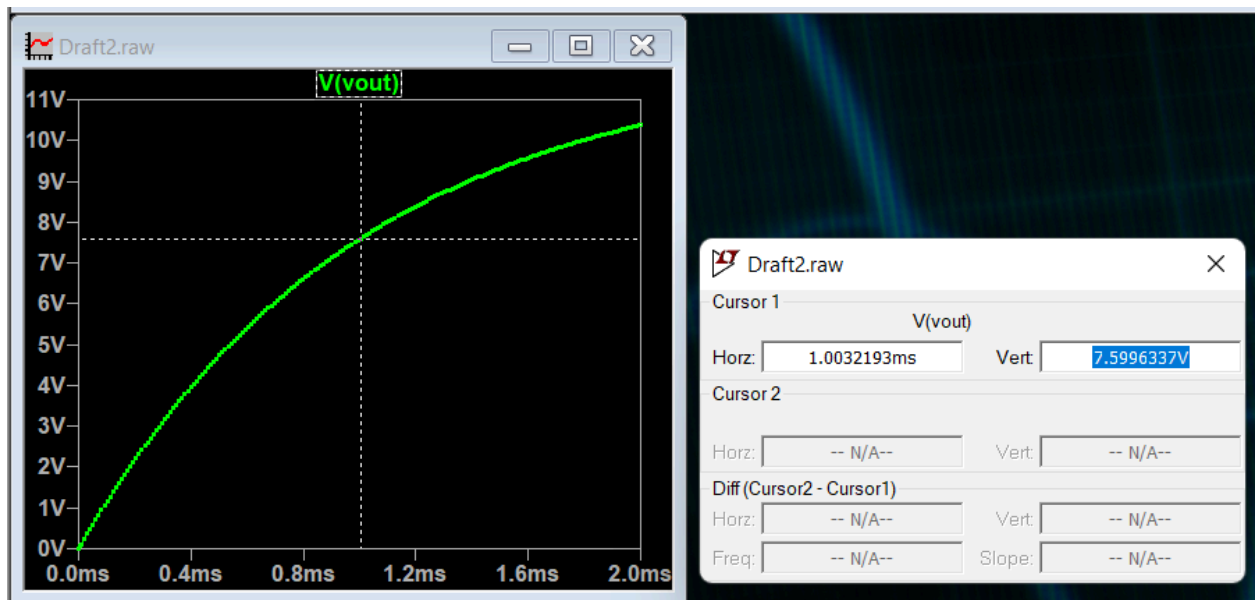

The measured time constant is 1.00 ms.

## Part 3: AC Analysis

Transient response plot:

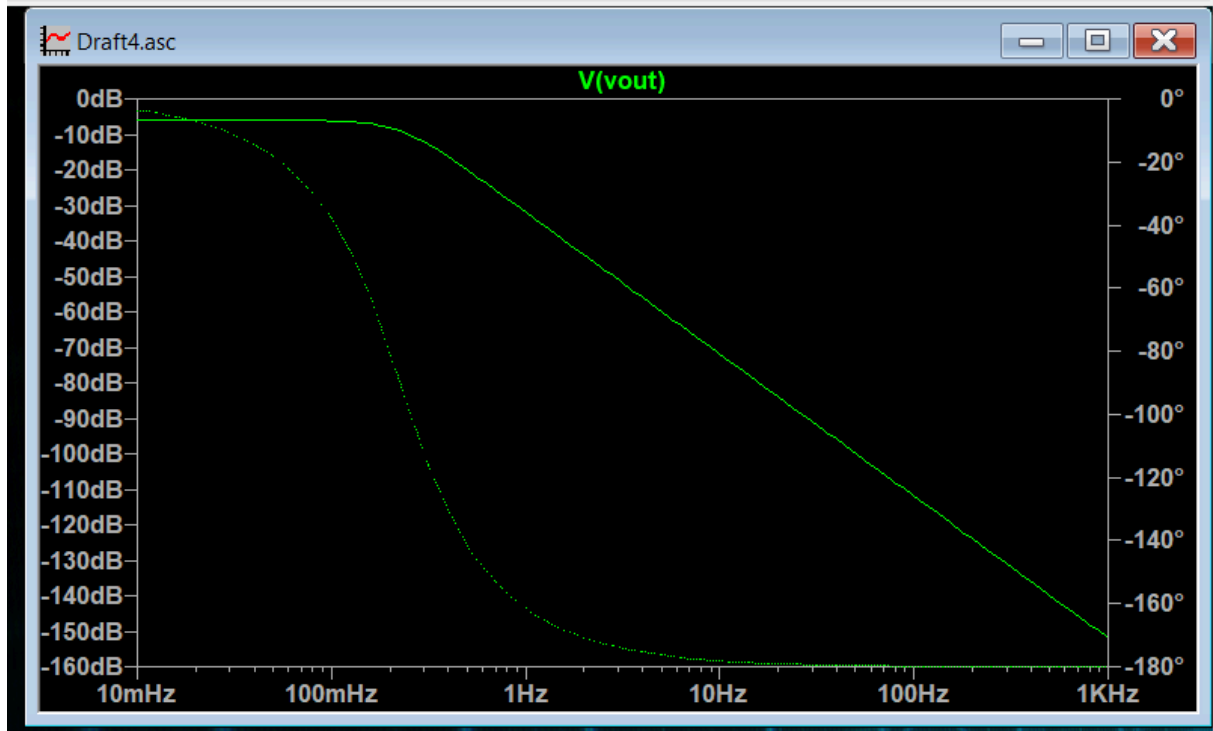

The solid trace is the gain, and the dashed trace is the phase shift.

At low frequencies, the gain is relatively high, and there is almost no phase shift. At high frequencies, the gain drops significantly, almost close to 0. The phase shift is close to 180 degrees.

This is because, at low frequencies, the inductor has a low impedance (acts as a wire), while the capacitor has a high impedance (acts as a break). The circuit essentially divides  $V_{in}$  by half. At high frequencies, the L and C properties flip.  $V_{out}$  is almost shorted to the ground.

